

$$1.1 \quad i = \frac{V}{R}$$

$$1.2 \quad i = -\frac{V}{R}$$

$$1.3 \quad i = \frac{V}{R} = \frac{6}{3} = 2 \text{ A}$$

$$1.4 \quad i = \frac{V}{R} = -\frac{6}{3} = -2$$

$$1.5 \quad V = V_0$$

$$1.6 \quad V = V_0$$

$$1.7 a) \quad V = \frac{R_2}{R_1 + R_2} V_0$$

$$b) \quad V = \left(\frac{R_1}{R_1 + R_2} + 1 \right) V_0 = V_0$$

$$1.8 \quad V_0 = -(V_1 + V_2) + (-V_5 - V_4) = -(6 - 4) + (-10 - 1) = -2 - 11 = -13 \text{ V}$$

$$1.9 a) \quad 4.5 \text{ V}$$

$$b) \quad 1.5 \text{ V}$$

$$1.10 a) \quad i_c = -1 \text{ A} + 2 \text{ A} - 4 \text{ A} = -3 \text{ A}$$

$$b) \quad i_d = 1 \text{ A} + 4 \text{ A} - 3 \text{ A} + 2 \text{ A} = 4 \text{ A}$$

$$c) \quad i_e = i_c = 1 \text{ A} + 5 i_c - 3 i_c + 3 \text{ A} = 4 \text{ A} + 2 i_c \Rightarrow i_c = -4 \text{ A}$$

$$1.12 \quad P = 1.0 \cdot 10^3 \text{ W}$$

$$a) \quad i = \frac{P}{V} = \frac{1 \cdot 10^3}{230} = 4.34 \text{ A}$$

$$b) \quad R = \frac{V}{i} = \frac{230}{4.34} = 52.9 \approx 53 \Omega$$

$$c) \quad S = \frac{365}{50} \cdot 1 = 7.3 \text{ k}\Omega$$

d)

1.14 Ingen. I a och b blir spänningen över R_b ej avlydd.

I c och d ligger en kortslutning parallellt med en spänningskälla.

$$1.15 \quad V_1 = -3 \text{ V} \quad V_2 = 5 \text{ V} \quad V_3 = 2 \text{ V}$$




$$V_4 = V_2 + V_1 - V_3 = 5 \text{ V} - 3 \text{ V} - 2 \text{ V} = 0 \text{ V}$$

$$V_5 = -4 \text{ V} - (V_4 - 2 \text{ V}) = -4 \text{ V} - (-2 \text{ V}) = -2 \text{ V}$$

1.16. Potential i nod 1 = 0.
 Nod 3: $5 - (-3) = 8V$

1.17
$$\begin{cases} i_1 = 5 \text{ mA} \\ i_2 = 15 \text{ mA} \\ i_3 = -9 \text{ mA} \\ i_5 = 0 \text{ mA} \end{cases} \quad \begin{aligned} i_1 + i_2 + i_3 + i_4 + i_5 &= 0 \\ \Rightarrow i_4 &= -i_1 - i_2 - i_3 - i_5 = \\ &= -5 - 15 + 9 - 0 = -7 \text{ mA} \end{aligned}$$

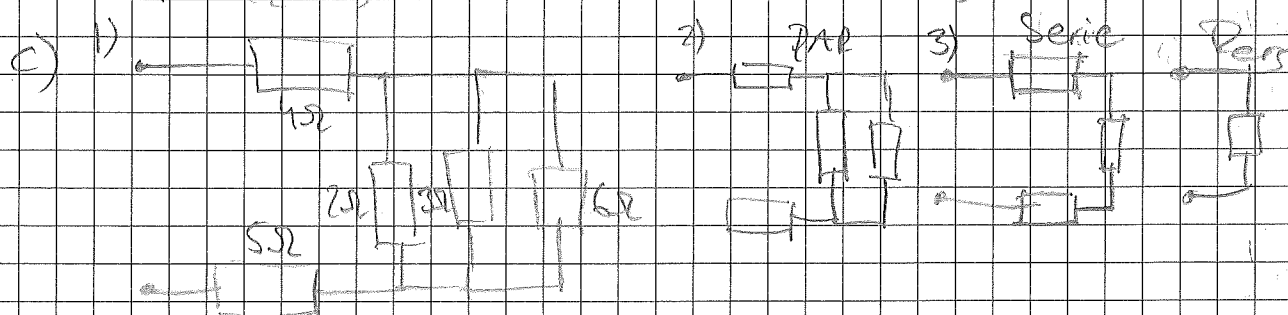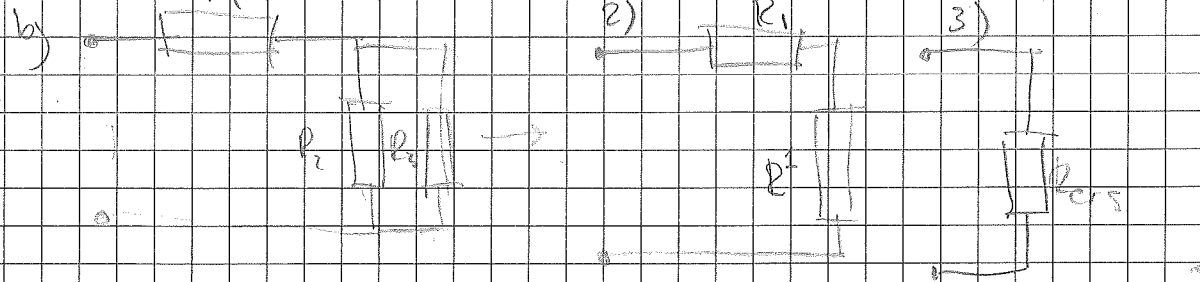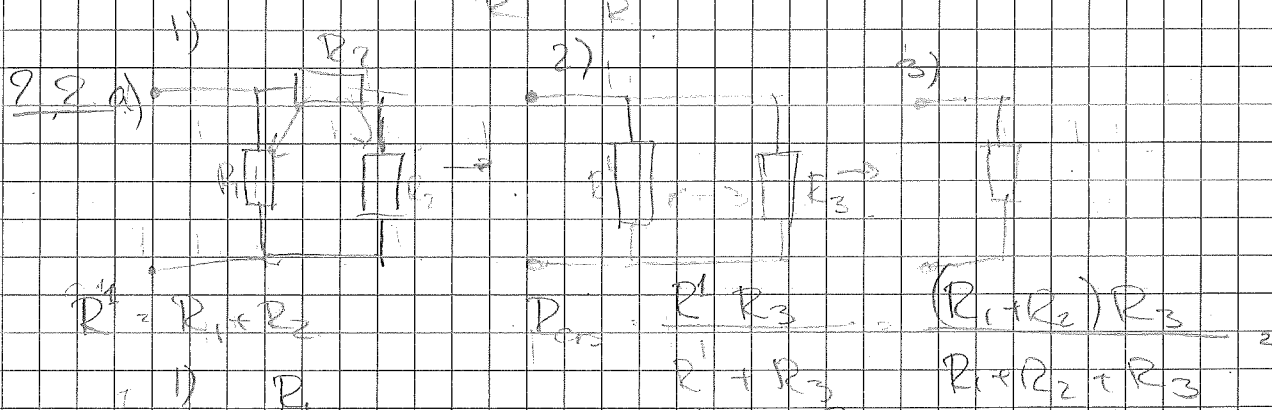1.18. $P = V_0 \cdot i \Rightarrow R = \frac{V}{i} \Rightarrow i = \frac{V}{R}$
 $\Rightarrow P = V_0 \cdot \frac{V_0}{R} = \frac{V_0^2}{R}$



1) $R' = \frac{6 \cdot 3}{6 + 3} = \frac{18}{9} = 2 \Omega$
 2) $R = \frac{2 \cdot 2}{2 + 2} = 1 \Omega$
 3) $R_{ens} = 4 \Omega + 5 \Omega + 1 \Omega = 10 \Omega$
 4) $R_{ens} = 4 \Omega + 5 \Omega + 1 \Omega = 10 \Omega$