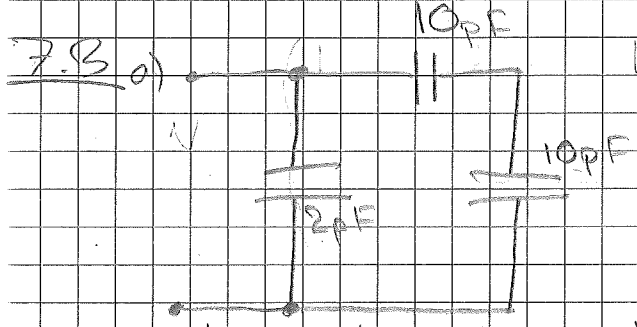


for $t \geq 0$:

$$i = C \frac{dv}{dt} = C \frac{d}{dt} (V_0 \sin(\omega t)) = C V_0 \omega \cos(\omega t)$$


$$p = v \cdot i = C V_0^2 \omega \sin(\omega t) \cos(\omega t)$$

$$w(t) = \frac{1}{2} C V^2 = \frac{1}{2} C V_0^2 \sin^2(\omega t)$$



$$a) \frac{1}{C'} = \frac{1}{10} + \frac{1}{10} \Rightarrow \frac{1}{C'} = \frac{1}{5} \Rightarrow C' = 5 \text{ pF}$$
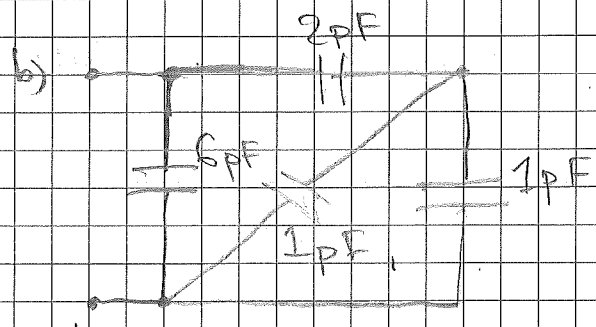
$$C_{\text{equiv}} = (5 + 2) \text{ pF} = 7 \text{ pF}$$



$$b) C' = 1 + 1 = 2 \text{ pF}$$

$$C'' = \frac{1}{2} + \frac{1}{2} = 1 \text{ pF}$$

$$C_{\text{equiv}} = 6 + 1 = 7 \text{ pF}$$

$$7.4 \quad C = \frac{\epsilon_0 A}{d}$$

$$W = \frac{\epsilon_0 A}{2d} N_0^2$$

$$Q = C \cdot N_0 = \frac{\epsilon_0 A}{d} N_0$$

Ny kapacitans: $C = \frac{\epsilon_0 A}{2d}$

$$\Rightarrow N_{ny} = \frac{\epsilon_0 A}{d} N_0 \cdot \frac{2d}{\epsilon_0 A} = 2N_0$$


$$W_{ny} = \frac{1}{2} \frac{\epsilon_0 A}{2d} 4N_0^2 = \frac{\epsilon_0 A}{d} N_0^2 = 2W_0$$

Mekaniskt arbete för att separera plattorna!


7.5



Vi antar längden l :

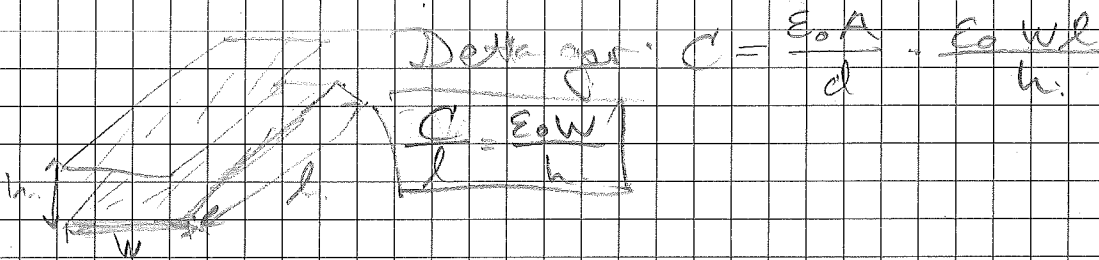

8.1

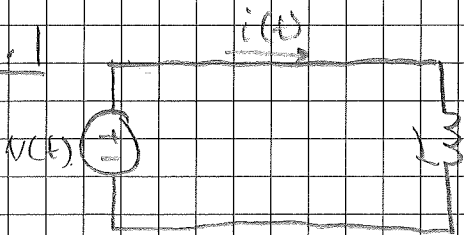

$$V(t) = V_0 \sin(\omega t) \quad t \geq 0$$

$$V(t) = 0 \quad t \leq 0$$


$$i(t) = \int V dt = \frac{1}{L} \int V_0 \sin(\omega t) dt = -\frac{V_0}{\omega L} \cos(\omega t)$$

$$i(t) = \begin{cases} -\frac{V_0}{\omega L} \cos(\omega t) & t > 0 \\ 0 & t \leq 0 \end{cases}$$

$$P = V \cdot i = -V_0 \sin(\omega t) \cdot \frac{V_0}{\omega L} \cos(\omega t) = -\frac{V_0^2}{\omega L} \sin(\omega t) \cos(\omega t)$$

$$P = \begin{cases} -\frac{V_0^2}{2\omega L} \sin(2\omega t) & t > 0 \\ 0 & t \leq 0 \end{cases}$$

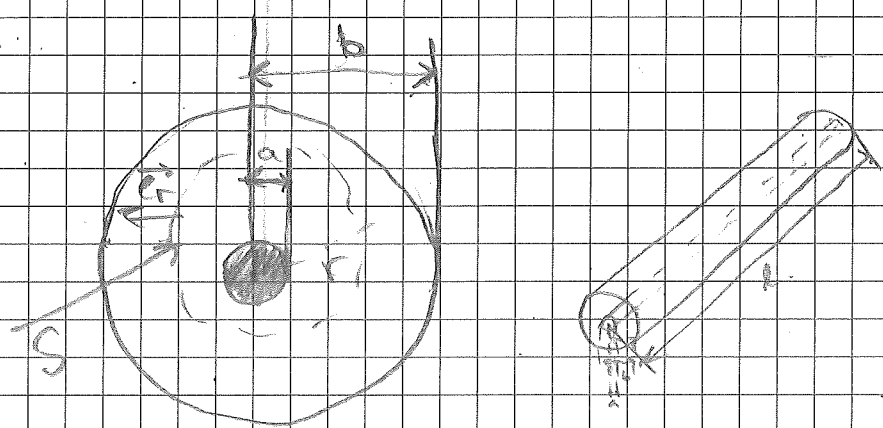
$$W(t) = \int P dt = \frac{1}{2} L \cdot \frac{V_0^2}{\omega L} \cos^2(\omega t) \Rightarrow W(t) = \begin{cases} \frac{1}{2} \frac{V_0^2}{\omega} \cos^2(\omega t) & t > 0 \\ 0 & t \leq 0 \end{cases}$$



Laddning på innerledare: q

Skapar en cylindergata S med radie r så att $a < r < b$

Symmetri ger följande fältbild:

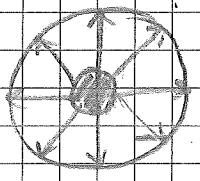

$\vec{E} = E(r)\vec{e}_r$. Gauss lag ger: $\epsilon_0 \oint_S \vec{E} \cdot \vec{e}_n dS = q \Rightarrow$

$$\frac{q}{\epsilon_0} = \oint_S \vec{E} \cdot \vec{e}_n dS = \int_0^l \int_0^{2\pi} E(r) \cdot \vec{e}_r \cdot \vec{e}_r r d\phi dz = 2\pi r l E(r)$$

Detta ger $E(r) = \frac{q}{2\pi r l \epsilon_0}$


$$V_a - V_b = \int_a^b \vec{E} \cdot d\vec{r} = \int_a^b \frac{q}{2\pi r l \epsilon_0} dr = \frac{q}{2\pi l \epsilon_0} \int_a^b \frac{1}{r} dr =$$

$$= \frac{q}{2\pi l \epsilon_0} \ln \frac{b}{a}. \text{ Detta ger } C = \frac{2\pi l \epsilon_0}{\ln \frac{b}{a}}$$

Kapacitansen / längdenhet blir då

$$\frac{C}{l} = \frac{2\pi \epsilon_0}{\ln(b/a)}$$

7.12

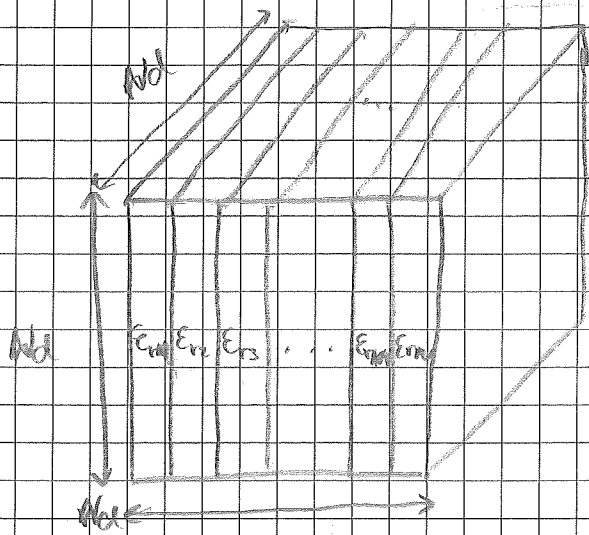

Variabelkapacitans:

$$C_n = \frac{\epsilon_0 \epsilon_n A U}{d_n} = \frac{\epsilon_0 \epsilon_n (Nd) U}{Nd}$$






a) Vinkelrett blir en summa av parallellkopplade kapacitanser.

$$C = \sum_{n=1}^N C_n = \sum_{n=1}^N \frac{\epsilon_0 \epsilon_n (Nd)^2}{Nd} = \epsilon_0 Nd \sum_{n=1}^N \epsilon_n$$

b) Parallellt blir en summa av seriekopplade kapacitanser:

$$C = \sum_{n=1}^N \frac{1}{C_n} = \sum_{n=1}^N \frac{Nd}{\epsilon_0 \epsilon_n (Nd)^2} = \frac{1}{\epsilon_0 Nd} \sum_{n=1}^N \frac{1}{\epsilon_n}$$

7.13

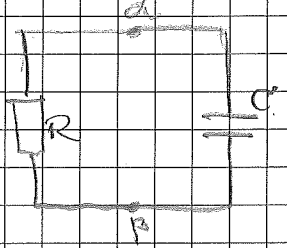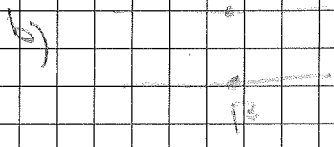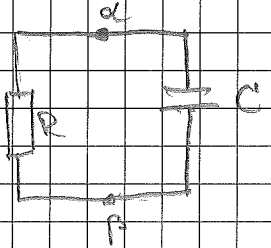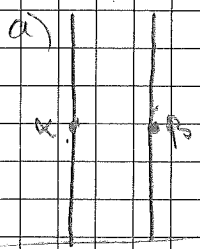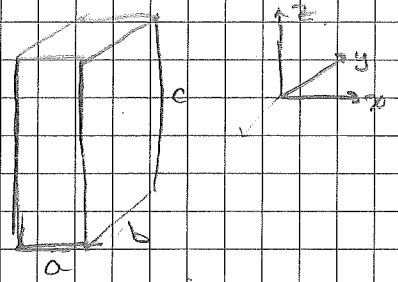

$$R = \frac{a}{\sigma bc}$$

$$C = \frac{\epsilon_0 \epsilon_r bc}{a}$$

$$R = \frac{c}{\sigma ab}$$

$$C = \frac{\epsilon_0 \epsilon_r ab}{c}$$

$a < b < c \Leftrightarrow$ $\left\{ \begin{array}{l} \text{Resistansen större i b} \\ \text{Kapacitansen större i a} \end{array} \right.$