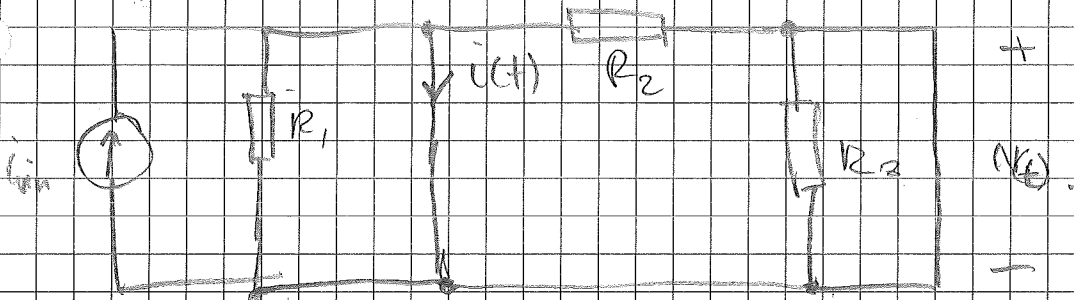



9.3.
$$i_{in} = \begin{cases} I_0 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

För $t = 0^+$ ersätter vi kondensatorerna med kortslutningar.



Delta ger $i(0^+) = I_0$; $U(0^+) = 0$.

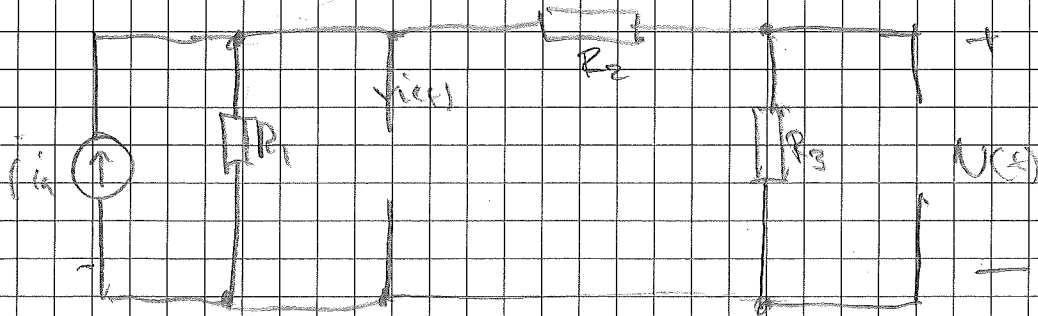För $t \rightarrow \infty$ ersätter vi kondensatorerna med avbrutt



$$\lim_{t \rightarrow \infty} i(t) = 0$$

Strömgrening:
$$i = \frac{R_3}{R_1 + R_2 + R_3} I_0 \stackrel{\lim_{t \rightarrow \infty}}{=} U(\infty) = \frac{R_1 R_3}{2 R_1 R_2 + R_3} I_0$$

Säuber $\frac{1}{RC} + \frac{1}{R_c C} = \alpha$

ger $N_c' + \alpha N_c = \frac{1}{RC} N_0 \Theta(t)$ Denna ODE löses med IF:

$$= N_c(t) e^{\alpha t} = \frac{1}{RC} \int N_0 e^{\alpha t} dt \Theta(t)$$

$$\Rightarrow N_c(t) = \left(\frac{1}{RC\alpha} N_0 + \beta e^{-\alpha t} \right) \Theta(t) \quad \text{BV } N_c(0) = 0 \text{ ger}$$

$$N_c(0) = 0 = \frac{1}{RC\alpha} N_0 + \beta \Rightarrow \beta = -\frac{1}{RC\alpha}$$

De är Ni:


$$N_c(t) = \frac{1}{RC} \cdot \left(\frac{1}{\frac{1}{RC} + \frac{1}{R_c C}} N_0 + \frac{1}{RC} \cdot \frac{1}{\frac{1}{RC} + \frac{1}{R_c C}} e^{-\left(\frac{1}{RC} + \frac{1}{R_c C}\right)t} \right)$$

$$= \left[\frac{1}{RC} \cdot \frac{1}{R_c C} - \frac{1}{R_c C} - \frac{R R_c C^2}{R(R_c + R)} \cdot \frac{R C R_c}{R + R_c} \right] =$$


$$= \frac{1}{RC} \cdot \frac{R_c}{R + R_c} N_0 + \frac{1}{RC} \cdot \frac{R C R_c}{R + R_c} e^{-\left(\frac{1}{RC} + \frac{1}{R_c C}\right)t}$$

$$= \frac{R_c}{R + R_c} N_0 + \frac{R_c}{R + R_c} e^{-\left(\frac{1}{RC} + \frac{1}{R_c C}\right)t}$$

Nast 1-2 m.issat

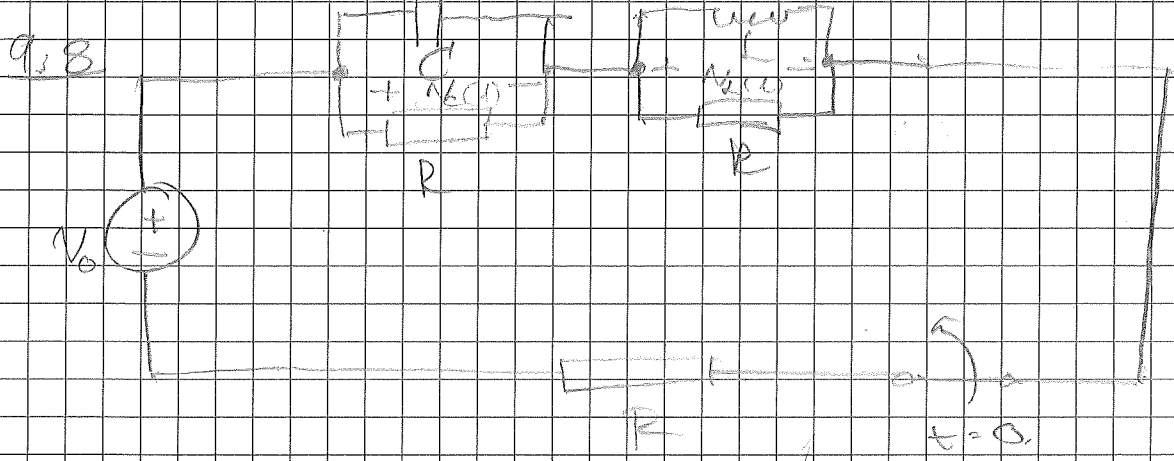

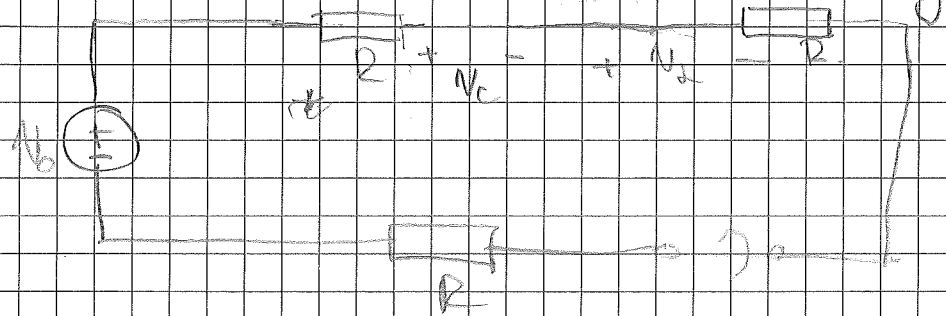a) ~~Leitstrom~~ / Kondensator: ~~Verbricht~~
 Spannung: ~~in~~ Kurzschluss



Delta gegen $V_c(0^-) = 0$

$$V_c = \frac{R}{2R} V_0 = \frac{V_0}{2} = V_c(0^-)$$



$V_c(t) = R \cdot i_c(t)$
 $V_c(t) = R \cdot i_c(t)$
 $= -RC \frac{dV_c(t)}{dt}$
 $\Rightarrow \begin{cases} V_c'(t) + \frac{1}{RC} V_c(t) = 0 \\ V_c(0) = \frac{V_0}{2} \end{cases}$

$\Rightarrow V_c(t) = \beta e^{-\frac{1}{RC}t}$

$V_c(0) = \frac{V_0}{2} = \beta \Rightarrow V_c(t) = \frac{V_0}{2} e^{-\frac{1}{RC}t}$

$V_2(t) \rightarrow R i_2 = L \frac{di_2}{dt}$

Ger $\rightarrow i_1' + \frac{R}{L} i_2 = 0$

BN: $i_1(0) = \frac{V_0}{2R}$

Si: $\begin{cases} i_1' + \frac{R}{L} i_2 = 0 \\ i_2(0) = \frac{V_0}{2R} \end{cases}$

$i_2(0) = \frac{V_0}{2R}$